

Circuits and Transforms

Sumanth N R

CONTENTS

1	Definitions	1
2	Laplace Transform	1
3	Initial Conditions	3

Abstract—This manual provides a simple introduction to Transforms

1 DEFINITIONS

1. The unit step function is

$$u(t) = \begin{cases} 1 & t > 0 \\ \frac{1}{2} & t = 0 \\ 0 & t < 0 \end{cases} \quad (1.1)$$

2. The Laplace transform of $g(t)$ is defined as

$$G(s) = \int_{-\infty}^{\infty} g(t)e^{-st} dt \quad (1.2)$$

2 LAPLACE TRANSFORM

1. In the circuit, the switch S is connected to position P for a long time so that the charge on the capacitor becomes $q_1 \mu C$. Then S is switched to position Q. After a long time, the charge on the capacitor is $q_2 \mu C$.


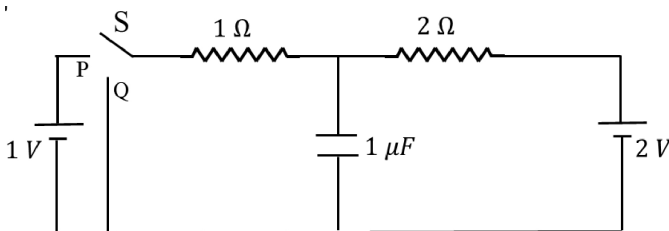


Fig. 2.1

2. Draw the circuit using latex-tikz.


Solution:

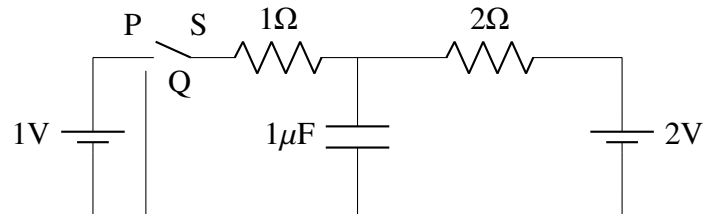

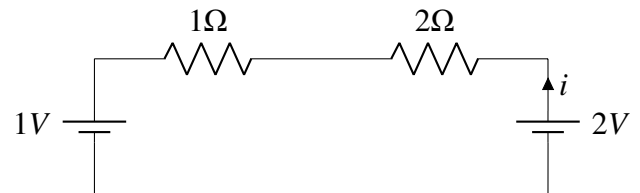3. Find q_1 .

Solution:

Current through the capacitor is 0 at steady state. So, current only flows in the outer loop.



$$i = \frac{(2 - 1) V}{(1 + 2) \Omega}$$

$$i = \frac{1}{3} A$$

Potential difference across the capacitor,

$$V_C = 2 - 2 \times \frac{1}{3} = \frac{4}{3} V$$

$$q_1 = CV_C$$

$$q_1 = 1\mu F \times \frac{4}{3} V$$

$$q_1 = \frac{4}{3} \mu C$$

4. Show that the Laplace transform of $u(t)$ is $\frac{1}{s}$ and find the ROC.

Solution:

By the definition of Laplace transform

$$u(t) \xrightarrow{\mathcal{L}} \int_{-\infty}^{\infty} u(t)e^{-st} dt = \int_0^{\infty} e^{-st} dt$$

$$= \frac{e^{-st}}{-s} \Big|_0^{\infty} = \frac{1}{s}$$

$\lim_{s \rightarrow \infty} e^{-st} = 0$ only when $Re(s) > 0$.

The ROC is $Re(s) > 0$.

5. Show that

$$e^{-at}u(t) \xleftrightarrow{\mathcal{H}} L \frac{1}{s+a}, \quad a > 0 \quad (2.1)$$

and find the ROC.

Solution:

By the definition of Laplace transform

$$\begin{aligned} e^{-at}u(t) &\xrightarrow{\mathcal{L}} \int_{-\infty}^{\infty} e^{-at}u(t)e^{-st}dt \\ &= \int_0^{\infty} e^{-(s+a)t}dt \\ &= \left. \frac{e^{-(s+a)t}}{-(s+a)} \right|_0^{\infty} = \frac{1}{s+a} \end{aligned}$$

$\lim_{s \rightarrow \infty} e^{-(s+a)t} = 0$ only when $\text{Re}(s+a) > 0$.

The ROC is $\text{Re}(s+a) > 0$ or $\text{Re}(s) > -a$.

6. Now consider the following resistive circuit transformed from Fig. 2.1 where

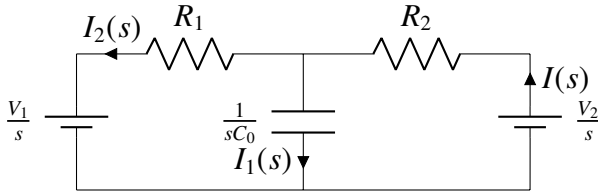


Fig. 2.2

$$u(t) \xleftrightarrow{\mathcal{H}} LV_1(s) \quad (2.2)$$

$$2u(t) \xleftrightarrow{\mathcal{H}} LV_2(s) \quad (2.3)$$

Find the voltage across the capacitor $V_{C_0}(s)$.

Solution:

Using the Transform from time domain to s-domain

$$\begin{aligned} V_1(s) &= \mathcal{L}(u(t)) = \frac{V_1}{s} \\ V_2(s) &= \mathcal{L}(2u(t)) = \frac{V_2}{s} \end{aligned}$$

Potential across the capacitor is $V_{C_0}(s)$ and the assuming bottom is grounded.

Applying KCL at the upper junction, we have,

$$\frac{V_{C_0}(s) - V_1(s)}{R_1} + \frac{V_{C_0}(s) - V_2(s)}{R_2} + \frac{V_{C_0}(s)}{\frac{1}{sC_0}} = 0$$

$$V_{C_0}(s) \left(\frac{1}{R_1} + \frac{1}{R_2} + sC_0 \right) = \frac{V_1(s)}{R_1} + \frac{V_2(s)}{R_2}$$

$$V_{C_0}(s) = \frac{V_1(s)R_2 + V_2(s)R_1}{R_1 + R_2 + sC_0R_1R_2}$$

$$V_{C_0}(s) = \frac{R_2 + 2R_1}{s(R_1 + R_2 + sC_0R_1R_2)}$$

after substitution.

7. Find $v_{C_0}(t)$. Plot using python.

Solution:

Factoring $V_{C_0}(s)$, we have

$$\begin{aligned} V_{C_0}(s) &= \left(\frac{1}{R_1 + R_2} \right) \left(\frac{(R_2 + 2R_1)}{s} - \frac{R_1R_2C_0(R_2 + 2R_1)}{R_1 + R_2 + sC_0R_1R_2} \right) \\ &= \left(\frac{R_2 + 2R_1}{R_1 + R_2} \right) \left(\frac{1}{s} - \frac{R_1R_2C_0}{R_1 + R_2 + sC_0R_1R_2} \right) \\ &= \left(\frac{R_2 + 2R_1}{R_1 + R_2} \right) \left(\frac{1}{s} - \frac{1}{\frac{1}{R_2C_0} + \frac{1}{R_1C_0} + s} \right) \end{aligned}$$

Applying inverse Laplace transform,

$$v_{C_0}(t) = \frac{R_2 + 2R_1}{R_1 + R_2} \left(u(t) - e^{-\left(\frac{1}{R_1C_0} + \frac{1}{R_2C_0}\right)t} u(t) \right)$$

Using the values $R_1 = 1 \Omega$, $R_2 = 2 \Omega$, $C_0 = 1 \mu F$, we get

$$v_{C_0}(t) = \frac{4}{3}u(t) \left(1 - e^{-1.5 \times 10^6 t} \right)$$

The following code yields $v_{C_0}(t)$.

```
wget https://github.com/Sigma1084/EE3900/
blob/master/cktsig/code/Ex2_plotVt.py
```


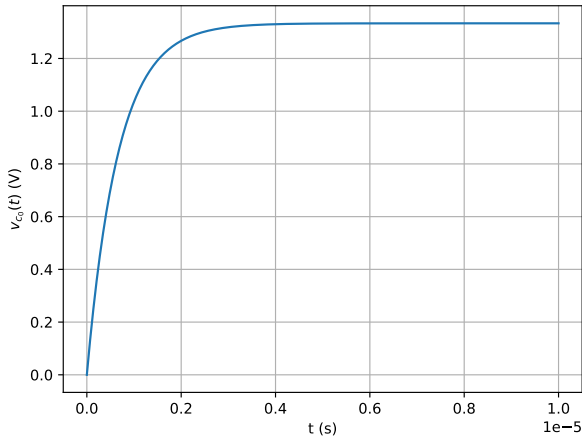


Fig. 2.3

8. Verify your result using ngspice.
9. Obtain Fig. 2.2 using the equivalent differential equation.

Solution:

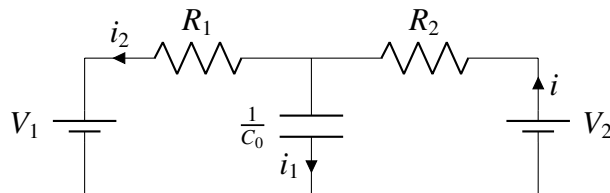

Using KVL on the left and right loops, we get

$$i_2(t) R_1 - V_1 - \int_0^t \frac{i_1(t)}{C_0} dt = 0$$

$$i(t) R_2 + V_2 + \int_0^t \frac{i_1(t)}{C_0} dt = 0$$

Taking the Laplace Transform after multiplying $u(t)$ in both equations,

$$\mathcal{L}\left(R_1 i_2(t)u(t) - V_1 u(t) - u(t) \int_0^t \frac{i_1}{C_0} dt\right) = 0$$

$$\mathcal{L}\left(R_2 i(t)u(t) + V_2 u(t) + u(t) \int_0^t \frac{i_1}{C_0} dt\right) = 0$$

Suppose $i(t)u(t) \xrightarrow{\mathcal{L}} I(s)$ and $Vu(t) \xrightarrow{\mathcal{L}} \frac{V}{s}$

$$\Rightarrow \mathcal{L}\left(u(t) \int_0^t \frac{i_1}{C_0} dt\right) = \frac{1}{sC_0} \mathcal{L}(u(t)i_1) = \frac{I_1(s)}{sC_0}$$

(Using the properties of Laplace Transform)


The above equations after transform

$$R_1 I_2(s) - \frac{V_1}{s} - \frac{I_1(s)}{sC_0} = 0$$

$$R_2 I(s) + \frac{V_2}{s} + \frac{I_1(s)}{sC_0} = 0$$

Now after applying the transformation, from time domain to s-domain, we replace the capacitor with an equivalent resistor of resistance $\frac{1}{sC_0}$ and replace I by $I(s)$, V by $\frac{V}{s}$

The equivalent s-domain circuit is now,

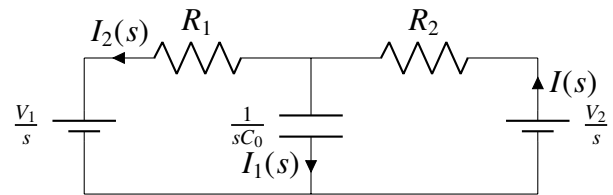

3 INITIAL CONDITIONS

1. Find q_2 in Fig. 2.1.
2. Draw the equivalent s -domain resistive circuit when S is switched to position Q. Use variables R_1, R_2, C_0 for the passive elements. Use latex-tikz.
3. $V_{C_0}(s) = ?$
4. $v_{C_0}(t) = ?$ Plot using python.
5. Verify your result using ngspice.
6. Find $v_{C_0}(0-)$, $v_{C_0}(0+)$ and $v_{C_0}(\infty)$.
7. Obtain the Fig. in problem 3.2 using the equivalent differential equation.