

# Circuits and Transforms

Sumanth N R

## CONTENTS

1	Definitions	1
2	Laplace Transform	1
3	Initial Conditions	3
4	Bilinear Transform	5

**Abstract**—This manual provides a simple introduction to Transforms

## 1 DEFINITIONS

1. The unit step function is

$$u(t) = \begin{cases} 1 & t > 0 \\ \frac{1}{2} & t = 0 \\ 0 & t < 0 \end{cases} \quad (1.1)$$

2. The Laplace transform of  $g(t)$  is defined as

$$G(s) = \int_{-\infty}^{\infty} g(t)e^{-st} dt \quad (1.2)$$

## 2 LAPLACE TRANSFORM

1. In the circuit, the switch S is connected to position P for a long time so that the charge on the capacitor becomes  $q_1 \mu C$ . Then S is switched to position Q. After a long time, the charge on the capacitor is  $q_2 \mu C$ .


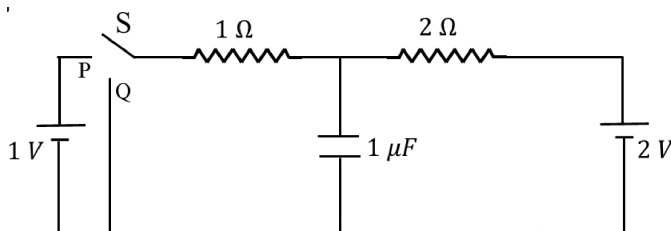


Fig. 2.1

2. Draw the circuit using latex-tikz.


**Solution:**

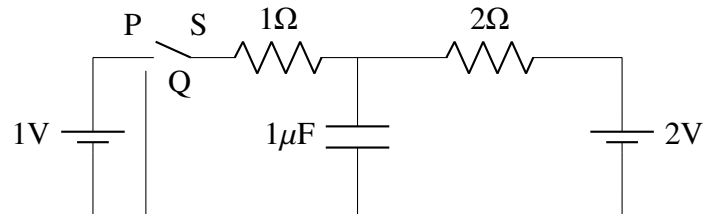

3. Find  $q_1$ .

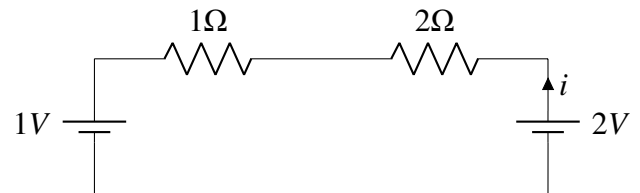**Solution:**

Current through the capacitor is 0 at steady state. So, current only flows in the outer loop.



$$i = \frac{(2 - 1) V}{(1 + 2) \Omega}$$

$$i = \frac{1}{3} A$$

Potential difference across the capacitor,

$$V_C = 2 - 2 \times \frac{1}{3} = \frac{4}{3} V$$

$$q_1 = CV_C$$

$$q_1 = 1\mu F \times \frac{4}{3} V$$

$$q_1 = \frac{4}{3} \mu C$$

4. Show that the Laplace transform of  $u(t)$  is  $\frac{1}{s}$  and find the ROC.

**Solution:**

By the definition of Laplace transform

$$u(t) \xrightarrow{\mathcal{L}} \int_{-\infty}^{\infty} u(t)e^{-st} dt = \int_0^{\infty} e^{-st} dt$$

$$= \left. \frac{e^{-st}}{-s} \right|_0^{\infty} = \frac{1}{s}$$

$\lim_{s \rightarrow \infty} e^{-st} = 0$  only when  $Re(s) > 0$ .

The ROC is  $Re(s) > 0$ .

5. Show that

$$e^{-at}u(t) \xleftrightarrow{\mathcal{H}} L \frac{1}{s+a}, \quad a > 0 \quad (2.1)$$

and find the ROC.

**Solution:**

By the definition of Laplace transform

$$\begin{aligned} e^{-at}u(t) &\xrightarrow{\mathcal{L}} \int_{-\infty}^{\infty} e^{-at}u(t)e^{-st}dt \\ &= \int_0^{\infty} e^{-(s+a)t}dt \\ &= \left. \frac{e^{-(s+a)t}}{-(s+a)} \right|_0^{\infty} = \frac{1}{s+a} \end{aligned}$$

$\lim_{s \rightarrow \infty} e^{-(s+a)t} = 0$  only when  $\text{Re}(s+a) > 0$ .

The ROC is  $\text{Re}(s+a) > 0$  or  $\text{Re}(s) > -a$ .

6. Now consider the following resistive circuit transformed from Fig. 2.1 where

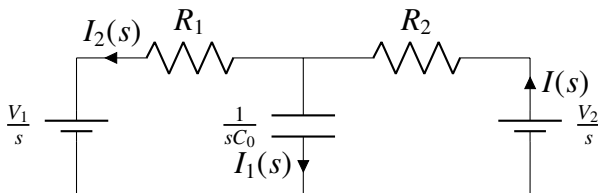


Fig. 2.2

$$u(t) \xleftrightarrow{\mathcal{H}} LV_1(s) \quad (2.2)$$

$$2u(t) \xleftrightarrow{\mathcal{H}} LV_2(s) \quad (2.3)$$

Find the voltage across the capacitor  $V_{C_0}(s)$ .

**Solution:**

Using the Transform from time domain to s-domain

$$\begin{aligned} V_1(s) &= \mathcal{L}(u(t)) = \frac{V_1}{s} \\ V_2(s) &= \mathcal{L}(2u(t)) = \frac{V_2}{s} \end{aligned}$$

Potential across the capacitor is  $V_{C_0}(s)$  and the assuming bottom is grounded.

Applying KCL at the upper junction, we have,

$$\frac{V_{C_0}(s) - V_1(s)}{R_1} + \frac{V_{C_0}(s) - V_2(s)}{R_2} + \frac{V_{C_0}(s)}{\frac{1}{sC_0}} = 0$$

$$V_{C_0}(s) \left( \frac{1}{R_1} + \frac{1}{R_2} + sC_0 \right) = \frac{V_1(s)}{R_1} + \frac{V_2(s)}{R_2}$$

$$V_{C_0}(s) = \frac{V_1(s)R_2 + V_2(s)R_1}{R_1 + R_2 + sC_0R_1R_2}$$

$$V_{C_0}(s) = \frac{R_2 + 2R_1}{s(R_1 + R_2 + sC_0R_1R_2)}$$

after substitution.

7. Find  $v_{C_0}(t)$ . Plot using python.

**Solution:**

Factoring  $V_{C_0}(s)$ , we have

$$\begin{aligned} V_{C_0}(s) &= \left( \frac{1}{R_1 + R_2} \right) \left( \frac{(R_2 + 2R_1)}{s} - \frac{R_1R_2C_0(R_2 + 2R_1)}{R_1 + R_2 + sC_0R_1R_2} \right) \\ &= \left( \frac{R_2 + 2R_1}{R_1 + R_2} \right) \left( \frac{1}{s} - \frac{R_1R_2C_0}{R_1 + R_2 + sC_0R_1R_2} \right) \\ &= \left( \frac{R_2 + 2R_1}{R_1 + R_2} \right) \left( \frac{1}{s} - \frac{1}{\frac{1}{R_2C_0} + \frac{1}{R_1C_0} + s} \right) \end{aligned}$$

Applying inverse Laplace transform,

$$v_{C_0}(t) = \frac{R_2 + 2R_1}{R_1 + R_2} \left( u(t) - e^{-\left(\frac{1}{R_1C_0} + \frac{1}{R_2C_0}\right)t} u(t) \right) \quad (2.4)$$

Using the values  $R_1 = 1 \Omega$ ,  $R_2 = 2 \Omega$ ,  $C_0 = 1 \mu F$ , we get

$$v_{C_0}(t) = \frac{4}{3}u(t) \left( 1 - e^{-1.5 \times 10^6 t} \right)$$

The following code yields  $v_{C_0}(t)$ .

```
wget https://github.com/Sigma1084/EE3900/
blob/master/cktsig/code/Ex2_plotVt.py
```

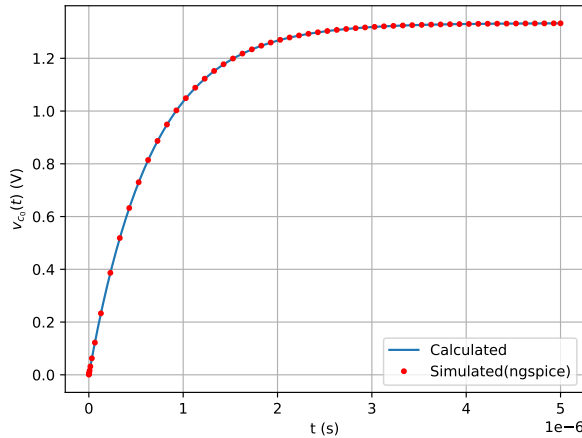



Fig. 2.3

8. Verify your result using ngspice. The following code yields  $v_{C_0}(t)$ . using ngspice

```
wget https://github.com/Sigma1084/EE3900/
blob/master/cktsig/code/Ex2.spice
```

9. Obtain Fig. 2.2 using the equivalent differential equation.

**Solution:**

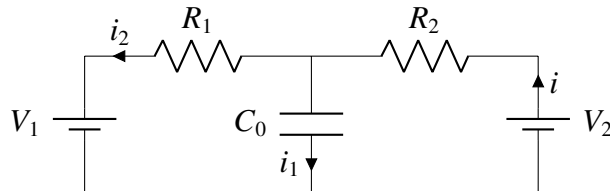

Using KVL on the left and right loops, we get

$$i_2(t) R_1 + V_1 - \int_0^t \frac{i_1(t)}{C_0} dt = 0 \quad (2.5)$$

$$-i(t) R_2 + V_2 - \int_0^t \frac{i_1(t)}{C_0} dt = 0 \quad (2.6)$$

Taking the Laplace Transform after multiplying  $u(t)$  in both equations,

$$\mathcal{L}\left(R_1 i_2(t)u(t) + V_1 u(t) - u(t) \int_0^t \frac{i_1}{C_0} dt\right) = 0$$

$$\mathcal{L}\left(-R_2 i(t)u(t) + V_2 u(t) - u(t) \int_0^t \frac{i_1}{C_0} dt\right) = 0$$

Suppose  $i(t)u(t) \xrightarrow{\mathcal{L}} I(s)$  and  $Vu(t) \xrightarrow{\mathcal{L}} \frac{V}{s}$

$$\Rightarrow \mathcal{L}\left(u(t) \int_0^t \frac{i_1}{C_0} dt\right) = \frac{1}{sC_0} \mathcal{L}(u(t)i_1) = \frac{I_1(s)}{sC_0}$$

(Using the properties of Laplace Transform)


The above equations after transform

$$R_1 I_2(s) + \frac{V_1}{s} - \frac{I_1(s)}{sC_0} = 0 \quad (2.7)$$

$$-R_2 I(s) + \frac{V_2}{s} - \frac{I_1(s)}{sC_0} = 0 \quad (2.8)$$

Now after applying the transformation, from time domain to s-domain, we replace the capacitor with an equivalent resistor of resistance  $\frac{1}{sC_0}$  and replace  $I$  by  $I(s)$ ,  $V$  by  $\frac{V}{s}$

The equivalent s-domain circuit is now,

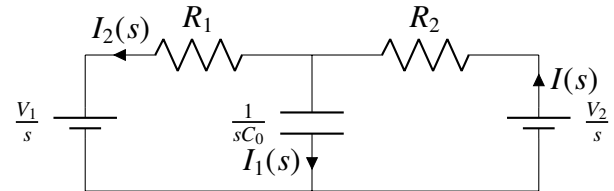

### 3 INITIAL CONDITIONS

1. Find  $q_2$  in Fig. 2.1

**Solution:**

Current through the capacitor is 0 in steady state. Since the current flows only in the outer loop, let the current in the outer loop be  $I$ .

$$I = \frac{2V}{(1+2)\Omega} = \frac{2}{3}A$$

So, the potential difference across the capacitor is

$$V_{C_0} = 2 - \left(\frac{2}{3} \times 2\right) = \frac{2}{3}V$$


$$q_2 = CV_{C_0}$$

$$q_2 = 1\mu C \times \frac{2}{3}V$$

$$q_2 = \frac{2}{3}\mu C$$

2. Draw the equivalent s-domain resistive circuit when S is switched to position Q. Use variables  $R_1, R_2, C_0$  for the passive elements. Use latex-tikz.

**Solution:**

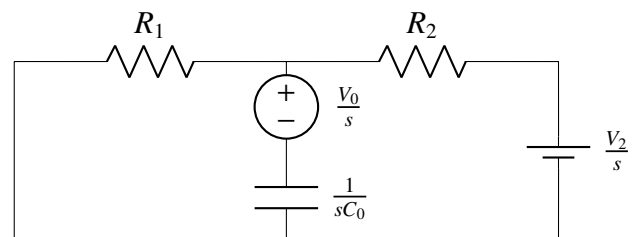

3.  $V_{C_0}(s) = ?$

**Solution:**

Applying KCL at the upper junction and assuming the bottom is grounded, we have,

$$\begin{aligned} \frac{V_{C_0}(s)}{R_1} + \frac{V_{C_0}(s) - \frac{V_2}{s}}{R_2} + \frac{V_{C_0}(s) - \frac{V_0}{s}}{\frac{1}{sC_0}} &= 0 \\ V_{C_0}(s) \left( \frac{1}{R_1} + \frac{1}{R_2} + sC_0 \right) &= \frac{V_2}{sR_2} + V_0C_0 \\ V_{C_0}(s) &= \frac{\frac{V_2}{sR_2} + V_0C_0}{\frac{1}{R_1} + \frac{1}{R_2} + sC_0} \\ V_{C_0}(s) &= V_0 \left( \frac{1}{\frac{1}{C_0} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + s} \right) \\ &+ \frac{V_2}{R_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)} \left( \frac{1}{s} - \frac{1}{\frac{1}{C_0} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + s} \right) \end{aligned}$$

4.  $v_{C_0}(t) = ?$  Plot using python.

**Solution:**

Applying inverse Laplace transform to  $V_{C_0}(s)$ , we have,

$$\begin{aligned} v_{C_0}(t) &= V_0 e^{-\left(\frac{1}{R_1} + \frac{1}{R_2}\right) \frac{t}{C_0}} u(t) \\ &+ \frac{V_2}{R_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)} \left( 1 - e^{-\left(\frac{1}{R_1} + \frac{1}{R_2}\right) \frac{t}{C_0}} \right) u(t) \end{aligned}$$

Substituting the values  $R_1 = 1, R_2 = 2, C_0 = 1\mu F, V_0 = \frac{4}{3}V, V_2 = 2V$

$$v_{C_0}(t) = \frac{2}{3} \left( 1 + e^{-(1.5 \times 10^6)t} \right) u(t) \quad (3.1)$$

The following code yields  $v_{C_0}(t)$ .

```
wget https://github.com/Sigma1084/EE3900/
blob/master/cktsig/code/Ex3_plotVt.py
```

5. Verify your result using ngspice. The following code yields  $v_{C_0}(t)$ . using ngspice

```
wget https://github.com/Sigma1084/EE3900/
blob/master/cktsig/code/Ex3.spice
```

6. Find  $v_{C_0}(0-), v_{C_0}(0+)$  and  $v_{C_0}(\infty)$ .

**Solution:**

Using the initial conditions, we have,

$$v_{C_0}(0-) = \frac{q_1}{C_0} = \frac{4}{3}V$$

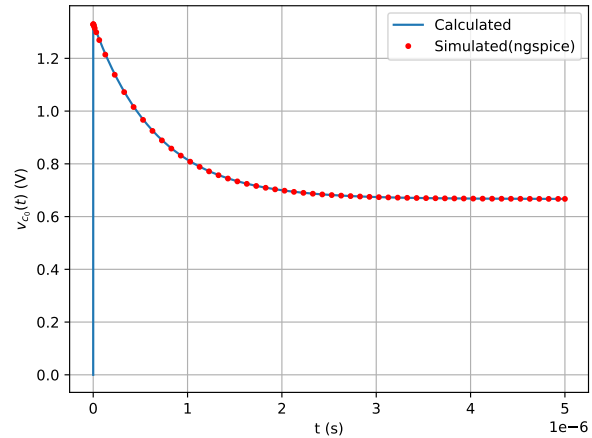


Fig. 3.1


Using (3.1), we have,

$$\begin{aligned} v_{C_0}(0+) &= \frac{2}{3} \left( 1 + e^{-(1.5 \times 10^6)0} \right) u(0+) = \frac{4}{3}V \\ v_{C_0}(\infty) &= \frac{2}{3} \left( 1 + e^{-(1.5 \times 10^6)\infty} \right) u(\infty) = \frac{2}{3}V \end{aligned}$$

7. Obtain the Fig. in problem 3.2 using the equivalent differential equation.

**Solution:**

Constructing the circuit,

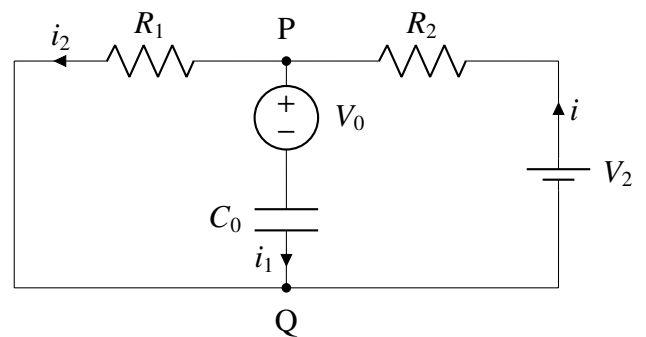

Using KVL on both the left and outer loops, we have

$$\begin{aligned} -i_2(t) R_1 + V_0 + \int_0^t \frac{i_1(t)}{C_0} dt &= 0 \\ -i(t) R_2 + V_2 - i_2(t) R_1 &= 0 \end{aligned}$$

Taking the Laplace Transform after multiplying  $u(t)$  in both equations,

$$\begin{aligned} \mathcal{L} \left( -R_1 i_2(t) u(t) + V_0 u(t) + u(t) \int_0^t \frac{i_1}{C_0} dt \right) &= 0 \\ \mathcal{L} (-R_2 i(t) u(t) + V_2 u(t) - R_1 i_2(t) u(t)) &= 0 \end{aligned}$$

Suppose  $i(t)u(t) \xrightarrow{\mathcal{L}} I(s)$  and  $Vu(t) \xrightarrow{\mathcal{L}} \frac{V}{s}$


$$\Rightarrow \mathcal{L}\left(u(t) \int_0^t \frac{i_1}{C_0} dt\right) = \frac{1}{sC_0} \mathcal{L}(u(t)i_1) = \frac{I_1(s)}{sC_0}$$

(Using the properties of Laplace Transform)

The above equations after transform

$$\begin{aligned} R_1 I_2(s) + \frac{V_0}{s} + \frac{I_1(s)}{sC_0} &= 0 \\ -R_2 I(s) + \frac{V_2}{s} - R_1 I_2(s) &= 0 \end{aligned}$$

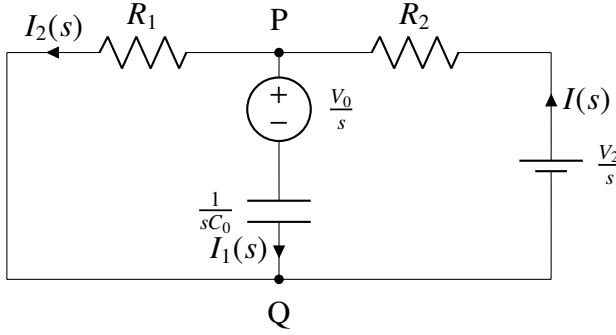
Now after applying the transformation, from time domain to s-domain, we replace the capacitor with an equivalent resistor of resistance  $\frac{1}{sC_0}$  and replace  $I$  by  $I(s)$ ,  $V$  by  $\frac{V}{s}$ , and hence we get,



#### 4 BILINEAR TRANSFORM

1. In Fig. 2.1, Consider the case when  $S$  is switched to  $Q$  right in the beginning. Formulate the differential equation.

**Solution:**

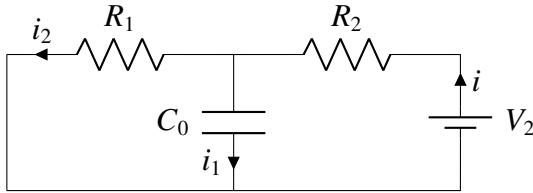

Special Case of (2.5), putting  $V_1 = 0$ , we get

$$i_2(t) R_1 - \int_0^t \frac{i_1(t)}{C_0} dt = 0 \quad (4.1)$$

$$V_2 - i(t) R_2 - i_2(t) R_1 = 0 \quad (4.2)$$

$$-i(t) R_2 + V_2 - \int_0^t \frac{i_1(t)}{C_0} dt = 0 \quad (4.3)$$

After transformation to s-domain, we get

$$\begin{aligned} R_1 I_2(s) - \frac{I_1(s)}{sC_0} &= 0 \\ -R_2 I(s) + \frac{V_2}{s} - R_1 I_2(s) &= 0 \end{aligned}$$

Differentiating w.r.t. time, we get,

$$\begin{aligned} R_1 \frac{di_2(t)}{dt} - \frac{i_1(t)}{C_0} &= 0 \\ R_2 \frac{di(t)}{dt} - \frac{i_1(t)}{C_0} &= 0 \end{aligned}$$

We need voltages in the final equation.

$$V_{C_0} = \frac{1}{C_0} q \Rightarrow \frac{dV_{C_0}}{dt} = \frac{1}{C_0} i_1$$

$$i(t) = i_1(t) + i_2(t) = C_0 \frac{dV_{C_0}}{dt} + \frac{1}{R_1} V_{C_0}$$

And this implies, equation (4.3) corresponds to

$$\begin{aligned} -\left(C_0 \frac{dV_{C_0}}{dt} + \frac{1}{R_1} V_{C_0}\right) R_2 + V_2 - V_{C_0} &= 0 \\ \frac{dV_{C_0}}{dt} + \frac{V_{C_0}}{C_0} \left(\frac{1}{R_1} + \frac{1}{R_2}\right) &= \frac{V_2}{C_0 R_2} \\ \frac{dV_{C_0}}{dt} + \frac{V_{C_0}}{\frac{C_0 R_1 R_2}{R_1 + R_2}} &= \frac{V_2}{C_0 R_2} \\ \Rightarrow \frac{dV_{C_0}}{dt} + \frac{V_{C_0}}{\tau} &= \frac{V_2}{C_0 R_2} \quad (4.4) \end{aligned}$$

Here,  $\tau = \frac{C_0 R_1 R_2}{R_1 + R_2}$  is the time constant of the circuit.

2. Find  $H(s)$  considering the output voltage at the capacitor.

**Solution:**

Recall that  $H(s) = \frac{V_{C_0}(s)}{V_2(s)}$

Using KCL at point P, after s-domain trans-

form, we have,

$$\begin{aligned} \frac{V_{C_0}(s)}{R_1} + \frac{V_{C_0}(s)}{\frac{1}{sC_0}} + \frac{V_{C_0}(s) - V_2(s)}{R_2} &= 0 \\ V_{C_0}(s) \left( \frac{1}{R_1} + sC_0 + \frac{1}{R_2} \right) &= \frac{V_2(s)}{R_2} \\ \frac{V_{C_0}(s)}{V_2(s)} = H(s) &= \frac{1}{R_2 \left( \frac{1}{R_1} + \frac{1}{R_2} + sC_0 \right)} \\ H(s) &= \frac{1}{C_0 R_2 \left( \frac{1}{\tau} + s \right)} \end{aligned} \quad (4.5)$$

3. Plot  $H(s)$ . What kind of filter is it?

**Solution:** The following code yields the graph  
Putting  $s = j\omega$  in the above equation, we can see that

$|H(j\omega)|$  is decreasing with increasing frequency.  
Clearly,  $H(s)$  is a low pass filter

4. Using trapezoidal rule for integration, formulate the difference equation by considering

$$y(n) = y(t)|_{t=n} \quad (4.6)$$

**Solution:**

From equation (4.4), putting  $V = V_{C_0}$  we have

$$\frac{dV}{dt} + \frac{V}{\tau} = \frac{V_2}{C_0 R_2}$$

where  $\tau = \frac{C_0 R_1 R_2}{R_1 + R_2}$  is the time constant.

Trapezoidal rule applied to  $y' = f(t, y)$  gives

$$y_{n+1} - y_n = \frac{1}{2} h \left( f(t_n, y_n) + f(t_{n+1}, y_{n+1}) \right)$$

where  $h = t_{n+1} - t_n$  is the step size.

Using the trapezoidal rule on (4.4), we get

$$\frac{v_{n+1} - v_n}{t_{n+1} - t_n} = \frac{1}{2} \left[ \frac{V_2(u(n) + u(n+1))}{C_0 R_2} - \frac{v_n + v_{n+1}}{\tau} \right]$$

Now, putting  $t_n = n \forall n$ , we get the difference equation

$$v_{n+1} - v_n + \frac{v_n + v_{n+1}}{2\tau} = \frac{V_2}{2C_0 R_2} (u(n) + u(n+1))$$

$$\begin{aligned} v_{n+1} \left( 1 + \frac{1}{2\tau} \right) - v_n \left( 1 - \frac{1}{2\tau} \right) &= \\ \frac{V_2}{2C_0 R_2} (u(n) + u(n+1)) \end{aligned} \quad (4.7)$$

where  $v_0 = 0$  is the initial condition.  
We get  $u(n)$  since  $V_2 = 0$  when  $t < 0$ .

5. Find  $H(z)$ .

**Solution:**

Taking  $\mathcal{Z}$ -Transform on (4.7), we get

$$zV(z) \left( 1 + \frac{1}{2\tau} \right) - V(z) \left( 1 - \frac{1}{2\tau} \right) = \frac{V_2}{2C_0 R_2} \frac{1 + z^{-1}}{1 - z^{-1}}$$

Now since  $V_2$  is constant at  $t > 0$ , we have

$$\mathcal{Z}(V_2) = \mathcal{Z}(V_2 u(n)) = \frac{V_2}{1 - z^{-1}}$$

We can substitute  $V_2$  in the above equation and since we know  $H(z) = \frac{V(z)}{V_2(z)}$ , we get

$$\begin{aligned} H(z) \left( \frac{2\tau - 1}{2\tau} \right) \left[ \frac{2\tau + 1}{2\tau - 1} - z^{-1} \right] &= \frac{1 + z^{-1}}{2C_0 R_2} \\ H(z) &= \frac{1}{C_0 R_2} \left( \frac{\tau}{2\tau - 1} \right) \frac{1 + z^{-1}}{\frac{2\tau + 1}{2\tau - 1} - z^{-1}} \\ H(z) &= \left( \frac{\tau}{C_0 R_2} \right) \frac{1 + z^{-1}}{(2\tau + 1) - (2\tau - 1)z^{-1}} \end{aligned} \quad (4.8)$$

$$|z| > 1 \text{ and } |z| > \frac{2\tau - 1}{2\tau + 1} \implies \text{ROC is } |z| > 1$$

6. How can you obtain  $H(z)$  from  $H(s)$ ?

**Solution:**

Using bilinear transform on (4.5),

setting  $s := \frac{2}{T} \frac{1 - z^{-1}}{1 + z^{-1}}$ , where  $T$  is the step size.

$$\begin{aligned} H(s) &= \frac{1}{R_2 \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{2}{T} \frac{1 - z^{-1}}{1 + z^{-1}} C_0 \right)} \\ H(s) &= \frac{1}{R_2 C_0 \left( \frac{1}{\tau} + \frac{2}{T} \frac{1 - z^{-1}}{1 + z^{-1}} \right)} \quad \left( \text{Since } \tau = \frac{C_0 R_1 R_2}{R_1 + R_2} \right) \\ H(s) &= \left( \frac{\tau}{C_0 R_2} \right) \frac{T(1 + z^{-1})}{T + Tz^{-1} + 2\tau - 2\tau z^{-1}} \\ H(s) &= \left( \frac{\tau}{C_0 R_2} \right) \frac{T(1 + z^{-1})}{(2\tau + T) - (2\tau - T)z^{-1}} \end{aligned}$$

Putting step size  $T = 1$ , we get  $H(z)$

Observe that

$$H(s) \Big|_{s=\frac{2}{T} \frac{1-z^{-1}}{1+z^{-1}}} = H(z)$$

7. Find  $v(n)$ . Verify using ngspice and the difference equation.

**Solution:**

We know that  $V(z) = H(z)V_2(z)$  and  $V_2(z) = \frac{V_2}{1-z^{-1}}$ . Using (4.8), we get

$$V(z) = \frac{1}{C_0 R_2 \left( \frac{1}{\tau} + \frac{2}{T} \frac{1-z^{-1}}{1+z^{-1}} \right)} \frac{V_2}{1-z^{-1}}$$

We can use Residue Theorem to find the inverse  $\mathcal{Z}$  transform

$$x(n) = \left[ \sum_{\text{Pole } z_i} \text{Residue of } X(z)z^{n-1} \text{ at } z_i \right]$$

$$\therefore v(n) = \sum_{\text{Pole } z_i} \left[ \frac{V_2}{C_0 R_2 \left( \frac{1}{\tau} + \frac{2}{T} \frac{1-z^{-1}}{1+z^{-1}} \right)} \frac{z^{n-1}}{1-z^{-1}} \right]_{z=z_i}$$

The only poles are  $z = 1$  and  $z = \frac{2\tau-T}{2\tau+T}$ . At  $z = 1$ , we get,

$$\begin{aligned} & \frac{V_2}{C_0 R_2 \left( \frac{1}{\tau} + \frac{2}{T} \frac{1-z^{-1}}{1+z^{-1}} \right)} \frac{z^{n-1}}{1-z^{-1}} \Big|_{z=1} \\ &= \frac{V_2}{C_0 R_2 \left( \frac{1}{\tau} + \frac{2}{T} \frac{1-z^{-1}}{1+z^{-1}} \right)} \frac{z^n}{1-z^{-1}} \Big|_{z=1} \\ &= \frac{V_2 \tau}{C_0 R_2} \end{aligned}$$

At  $z = \frac{2\tau-T}{2\tau+T}$ , we get,

$$\begin{aligned} & \frac{V_2}{C_0 R_2} \frac{\left( z - \frac{2\tau-T}{2\tau+T} \right) z^{n-1}}{\left( \frac{1}{\tau} + \frac{2}{T} \frac{1-z^{-1}}{1+z^{-1}} \right) 1-z^{-1}} \Big|_{z=\frac{2\tau-T}{2\tau+T}} \\ &= \frac{V_2 T \tau}{C_0 R_2} \frac{\left( z - \frac{2\tau-T}{2\tau+T} \right) z^{n-1} (1+z^{-1})}{(2\tau+T - (2\tau-T)z^{-1}) 1-z^{-1}} \Big|_{z=\frac{2\tau-T}{2\tau+T}} \\ &= \frac{V_2}{C_0 R_2} \cdot \frac{\tau T z^n}{2\tau+T} \cdot \frac{1+z^{-1}}{1-z^{-1}} \Big|_{z=\frac{2\tau-T}{2\tau+T}} \\ &= \frac{V_2}{C_0 R_2} \cdot \frac{\tau T z^n}{2\tau+T} \cdot \frac{\frac{2\tau-T}{2\tau+T} + 1}{\frac{2\tau-T}{2\tau+T} - 1} \\ &= \frac{V_2}{C_0 R_2} \cdot \frac{\tau T z^n}{2\tau+T} \cdot \frac{4\tau}{-2T} \\ &= -\frac{V_2 \tau}{C_0 R_2} \cdot \frac{2\tau}{2\tau+T} \cdot z^n \\ &= -\frac{V_2 \tau}{C_0 R_2} \cdot \frac{1}{1 + \frac{T}{2\tau}} \cdot \left( \frac{2\tau-T}{2\tau+T} \right)^n \end{aligned}$$

Hence, we get

$$v(n) = \frac{V_2 \tau}{C_0 R_2} \left[ 1 - \frac{1}{1 + \frac{T}{2\tau}} \cdot \left( \frac{2\tau-T}{2\tau+T} \right)^n \right] u(n)$$

ROC is  $z > 1$

Taking the sampling frequency,  $T$  to be low and plugging in values, we get

$$y(n) \approx \frac{2}{3} \left( 1 - \frac{1 - 7.5 \times 10^5 n}{1 + 7.5 \times 10^5 n} \right) u(n)$$

Now, considering the Laplace Transform

$$V(s) = H(s) \cdot V_2(s) = \frac{5 \times 10^5}{s + 1.5 \times 10^6} \frac{2}{s}$$

Taking partial fractions, we get

$$V(s) = \frac{10^6}{1.5 \times 10^6} \left( \frac{1}{s} - \frac{1}{s + 1.5 \times 10^6} \right)$$

Taking the inverse Laplace Transform, we get

$$y(t) = \frac{2}{3} \left( 1 - e^{-1.5 \times 10^6 t} \right) u(t)$$

with ROC  $s > 0$

Now, approximating,

$$e^{-1.5 \times 10^6 t} = \frac{e^{-0.75 \times 10^6 t}}{e^{0.75 \times 10^6 t}} \approx \frac{1 - 7.5 \times 10^5 t}{1 + 7.5 \times 10^5 t} \quad \text{when } t \ll 10^{-6}$$

$$\Rightarrow y(t) \approx \frac{2}{3} \left( 1 - \frac{1 - 7.5 \times 10^5 t}{1 + 7.5 \times 10^5 t} \right) u(t)$$

We just proved that  $y(n) = y(t)|_{t=n}$ . And hence, verified the correctness of Bilinear Transform. The following code yields the graph

```
wget https://github.com/Sigma1084/EE3900/
blob/master/cktsig/code/Ex4_plot.py
```

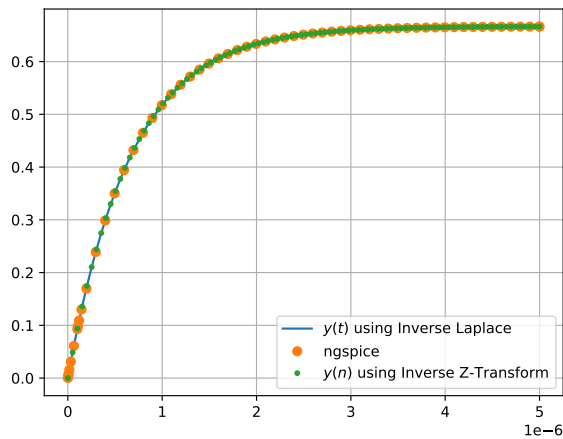


Fig. 4.1

8. Find  $y(n)$  using the difference equation and verify

**Solution:**

Using the equation (4.7), we get

$$v_{n+1} \left( 1 + \frac{1}{2\tau} \right) - v_n \left( 1 - \frac{1}{2\tau} \right) = \frac{V_2}{2C_0 R_2} (u(n) + u(n+1))$$

And hence, we have

$$v_{n+1} = v_n \left( \frac{2\tau - 1}{2\tau + 1} \right) + \left( \frac{2\tau}{2\tau + 1} \right) \frac{V_2}{2C_0 R_2} (u(n) + u(n+1))$$

Since  $v_0 = 0$  and  $\forall n \geq 0$ ,  $u(n) + u(n+1) = 2$ , we can solve the linear difference equation.

For all  $n \geq 0$

$$v_{n+1} = -\frac{7.5 \times 10^5 - 1}{7.5 \times 10^5 + 1} v_n + \frac{10^6}{7.5 \times 10^5 + 1}$$

Write  $v_{n+1} = av_n + b$

$$v_1 = av_0 + b = b$$

$$v_2 = av_1 + b = ab + b = b(a + 1)$$

$$v_3 = av_2 + b = a^2b + ab + b = b(a^2 + 2a + 1)$$

$\vdots$

$$v_n = a^n v_0 + b \sum_{k=0}^{n-1} a^k = b \left( \frac{a^n - 1}{a - 1} \right)$$

$$\Rightarrow v_n = \frac{10^6}{2 \times 7.5 \times 10^5} \times \left( 1 - \left( -\frac{7.5 \times 10^5 - 1}{7.5 \times 10^5 + 1} \right)^n \right)$$

$$\Rightarrow v_n = \frac{2}{3} \left( 1 - \left( \frac{1 - 7.5 \times 10^5}{1 + 7.5 \times 10^5} \right)^n \right) u(n)$$

Notice that this is the same equation we got from earlier